

**PARUL UNIVERSITY**  
**FACULTY OF ENGINEERING & TECHNOLOGY**  
**B.Tech., Summer 2016 - 17 Examination**

**Semester: 3**  
**Subject Code: 03107203**  
**Subject Name: Digital Electronics**

**Date: 24/06/2017**  
**Time: 10 am to 1 pm**  
**Total Marks: 100**

**Instructions:**

1. Attempt all questions from each section.
2. Figures to the right indicate full marks.
3. Make suitable assumptions wherever necessary.
4. Write section-A, section-B on separate answer sheets.

**SECTION: A**

**Q:1** (a) Convert Decimal Number 250.5 to base 3 and base 7. (05)

**Q:1** (b) Find 1's and 2's complement of following binary nos.  $(10001)_2$ ,  $(101011)_2$  (05)

**Q:2** (a) Implement Boolean function  $F = x y + x' y' + y' z$  with OR & NOT gates. (07)

**Q:2** (b) Define the Integrated Circuit and briefly explain SSI, MSI, LSI and VLSI. (07)

**OR**

**Q:2** (b) Give classification of Logic Families and compare CMOS and TTL Families (07)

**Q:3** (a) Reduce the expression: (07)

1.  $A+B(AC+(B+C')D)$       2.  $(A+(BC)')'(AB'+ABC)$

**Q:3** (b) Design combinational circuits for a full adder. (06)

**OR**

**Q:3** (b) What is meant by multiplexer? Explain with diagram and truth table the Operation of 4-to-1 line multiplexer. (06)

**Q:4** (a) Simplify Boolean function (07)

$$F = A'B'D' + A'CD + A'BC$$

$$d = A'BC'D + ACD + AB'D' \text{ Where "d" indicates Don't care conditions.}$$

**Q:4** (b) Simplify Boolean function using K-map and draw logic diagram for simplified Boolean function:  $F(w,x,y,z) = \Sigma (0,1,2,4,5,6,8,9,12,13,14)$  (06)

**SECTION: B**

**Q:1** (a) Explain operation of Master –Slave J-K Flip-Flop. (05)

**Q:1** (b) Write excitation table of all types of flip-Flops (05)

**Q:2** (a) Explain in detail operation of 4 bit Shift Register for all 4 operating modes. (07)

**Q:2** (b) Compare PLA and PAL. (06)

**OR**


**Q:2** (b) Write a short note on FPGA. (06)

**Q:3** (a) Design a counter with the following binary sequence: 0,1,3,7,6,4, and repeat. (Use T flip-flop) (07)

**Q:3** (b) A sequential circuit has one input (X) and one output (Z). The circuit examines groups of four consecutive inputs and produces an output  $Z = 1$  if the input sequence 0101 or 1001 occurs. The circuit resets after every four inputs. Find the Mealy state graph. (06)

**OR**

 **Q:3** (b) Design Sequential Circuit using D flip flop for given state diagram. (06)



**Q:4** (a) Derive the state graph using elimination of redundant state method. (Take appropriate Example.) (07)

**Q:4** (b) What is the basic difference between synchronous and asynchronous counter? Describe synchronous 3-bit up counter. (07)