

Parul Institute of Engineering & Technology

Engineering Department

ASSIGNMENT-3

Subject Name: DIGITAL ELECTRONICS

Subject Code: 203105201

(Chapter-3-Combinational Logic)

- 1.** Design the Combinational Circuits for Binary to Gray Code Conversion. **2.** Explain Design Procedure for Combinational Circuit & Difference between Combinational Circuit & Sequential Circuit.
- 3.** Construct 4*16 Decoder with help of 2*4 Decoder.
- 4.** Discuss 4 bit BCD Adder in Detail.
- 5.** Explain 4 bit Magnitude Comparator.
- 6.** Explain common cathode types seven segments displays.
- 7.** Design combinational circuits for a full adder.
- 8.** Design a full-adder with two half-adders and an OR gate
- 9.** Design a combinational circuit for a full subtractor.
- 10.** Design combinational circuits for a half adder.
- 11.** Design a combinational circuit for a half subtractor.
- 12.** Design a combinational circuit whose input is a four bit number and whose Output is the 2's complement of the input number.
- 13.** Draw symbol and truth table for four input EX-OR and EX-NOR gate. Explain NAND and NOR as an universal gate.
- 14.** Design BCD to Excess-3 code converter using minimum number of NAND gates.
- 15.** Simplify Boolean function $F(w,x,y,z) = \sum (0,1,2,4,5,6,8,9,12,13,14)$ using K-map