

# Parul Institute of Engineering & Technology

## Electronics & Communication Engineering Department

### ASSIGNMENT-2

**Subject Name: DIGITAL ELECTRONICS**

**Subject Code: 203105201**

**(Chapter-2- Minimization Techniques)**

1. Given Boolean function  
 $F = x y + x' y' + y' z$ 
  - a. Implement it with only OR & NOT gates
  - b. Implement it with only AND & NOT gates
2. Express following Function in Product of Maxterms  
 $F(x,y,z) = (xy + z)(y + xz)$
3. Explain briefly : SOP & POS , minterm & maxterm , canonical form , (05)  
propagation delay, fan out
4. What is the principle of Duality Theorem?
5. Explain briefly: standard SOP and POS forms.
6. What are Minterms and Maxterms?
7. Define: Noise margin , Propagation delay
8. Reduce the expression:  
a.  $A+B(AC+(B+C')D)$       b.  $(A+(BC)')'(AB'+ABC)$
9. Define : Integrated Circuit and briefly explain SSI, MSI, LSI and VLSI
10. Draw the logic symbol and construct the truth table for each of the .  
[1] Two input NAND gate      [2] Three input OR gate  
[3] Three input EX-NOR gate      [4] NOT gate
11. Give classification of Logic Families and compare CMOS and TTL Families
12. Demonstrate by means of truth tables the validity of the following Theorems of Boolean algebra
  - (i) De Morgan's theorems for three variables
  - (ii) The Distributive law of + over-
13. Express the following functions in sum of min terms and product of max terms:
  - a.  $F(A,B,C,D) = D(A'+B) + B'D$
  - b.  $F(A,B,C) = (A'+B)(B'+C)$
  - c.  $F(x,y,z) = 1$