

PARUL UNIVERSITY
FACULTY OF ENGINEERING & TECHNOLOGY
B.Tech. Winter 2016 - 17 Examination

Semester: 3
Subject Code: 03107203
Subject Name: Digital Electronics

Date: 19-12-2016
Time: 10:00AM to 01:00PM
Total Marks: 100

Instructions:

1. Attempt all questions from each section.
2. Figures to the right indicate full marks.
3. Make suitable assumptions wherever necessary.
4. Write section-A, section-B on separate answer sheets.

SECTION: A

Q:1 (a) Convert following Numbers as directed (05)

(i) $(101001011)_2 = ()_{10}$ (ii) $(225.225)_{10} = ()_8$

(iii) $(7654)_{10} = ()_{BCD}$ (iv) $(F28)_{16} = ()_{10}$ (v) $(414)_8 = ()_{16}$

Q:1 (b) (1) Perform subtractions with the following binary numbers using 2's complement (05)

(i) $10010 - 10011$ (ii) $100 - 110000$

(2) Find 10's complement of following nos. (i) 3405.65, (ii) 87.76

Q:2 (a) Explain De Morgan's theorems in detail. (07)

Q:2 (b) Construct 4*16 Decoder with help of 2*4 Decoder. (07)

OR

Q:2 (b) Simplify the function using K-Map and implement with only NOR gates (07)

$F(w,x,y,z) = m(1, 3, 7, 11, 15)$ with don't care conditions

$d(w,x,y,z) = m(0, 2, 5)$

Q:3 (a) Design Combinational Circuits for Binary to Gray Code Conversion (07)

Q:3 (b) Reduce given expression by using Quine McClusky Method to find Prime Implicants (06)

$F(a,b,c,d) = m(0,1,2,5,6,7,8,9,10,14)$

OR

Q:3 (b) Design BCD to Excess-3 code converter using minimum number of NAND gates. (06)

Q:4 (a) Explain Half Adder and Full Adder in detail and also Implement a full adder circuit (07)
 using a decoder and OR gates.

Q:4 (b) What is meant by multiplexer? Explain with logic diagram and truth table, Operation (06)
 of 8-to-1 line multiplexer

SECTION: B

Q:1 (a) Draw and explain the working of following flip-flops (05)

(i) Clocked RS (ii) T-flip-flop

Q:1 (b) Explain J-K flip-flop with necessary logic diagram, state equation and Truth table. (05)
 How JK flip-flop is the refinement of RS flip-flop?

Q:2 (a) Design a counter with the following sequence: 0, 4, 2, 1, 6 and repeat. Use JK (07)
 flip-flop.

Q:2 (b) List out 4 different operating modes of Shift Register. And explain in detail SISO (06)
 & PISO modes.

OR


Q:2 (b) Define: State table, State equation, State diagram, input & output equations. (06)

Q:3 (a) Define Odd and Even Parity and Consider 7 digit data as below and convert that data (07)
 in to Odd Parity Sequence and Even Parity Sequence

(i) 0011010 (ii) 0111111 (iii) 0110111 (iv) 0000100 (v) 1010101

Q:3 (b) Design Sequence Detector for below State Graph

(06)

 

OR

(b) Design a 4 bit Binary Counter using D flip flop.

(06)

Q:4 (a) Compare RAM , ROM and EPROM and list the different types of PLDs.

(07)

Q:4 (b) Reduce the following state table to a minimum number of states and draw reduced state graph.

(07)

Input Sequence	Present state	Next state		Present Output	
		X=0	X=1	X=0	X=1
reset	A	B	C	0	0
0	B	D	E	0	0
1	C	F	G	0	0
00	D	H	I	0	0
01	E	J	K	0	0
10	F	L	M	0	0
11	G	N	P	0	0
000	H	A	A	0	0
001	I	A	A	0	0
010	J	A	A	0	1
011	K	A	A	0	0
100	L	A	A	0	1
101	M	A	A	0	0
110	N	A	A	0	0
111	P	A	A	0	0